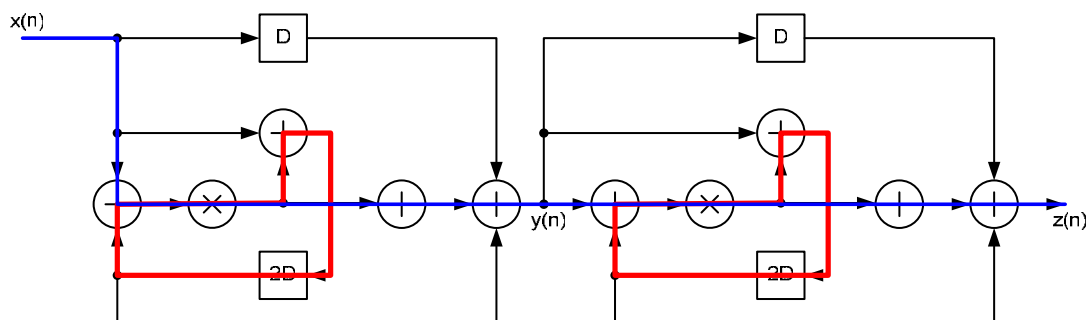


# DSP in VLSI Design


## Homework (IV)

### Retiming Reference Answer

1. Consider the wave digital filter shown below. Assume that each multiply operation requires 20 ns and each add operation required 10 nsec.
  - (a) Calculate the iteration period bound of this filter by inspection.
  - (b) Where is the critical path?
  - (c) Manually pipeline and/or retime this filter to achieve a critical path equal to the iteration period bound.




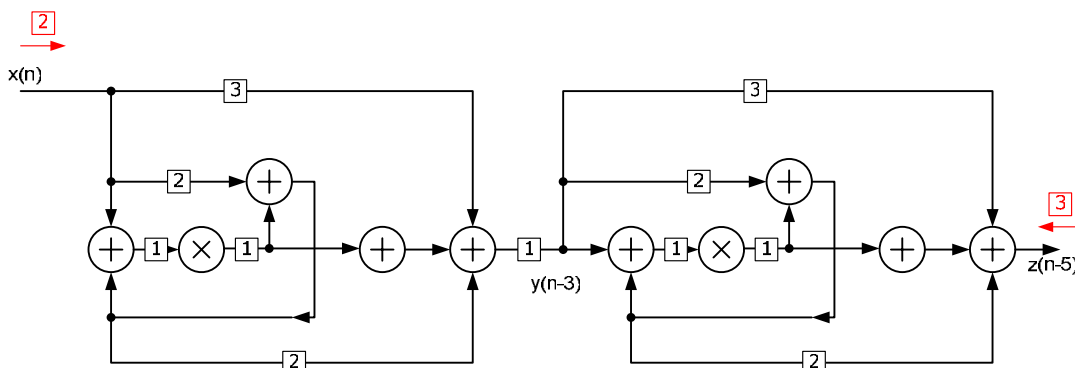- (a) Iteration bound: Red circle, 2 adders & 1 multiplier, 2 Delays,  $2 \times 10 + 1 \times 20 = 40$   
Iteration bound =  $40/2 = 20$  ns
- (b) Critical path: Blue line, 6 adders & 2 multipliers,  $6 \times 10 + 2 \times 20 = 100$   
Critical path = 100 ns
- (c) Pipeline from  $x(n)$  with 2 delays, from  $z(n)$  with 3 delays. After retiming, the result is shown below.




 2. Consider the IIR filter DFG shown in below. Assume that addition and multiplication require 1 and 2 u.t., respectively.

- By inspection, calculate the iteration bound.
- Compute the critical path time of the circuit.
- Pipeline and/or retime this system to achieve a critical path of 2 u.t. Do this by inspection (manually).
- Pipeline and/or retime this system to achieve sample period of 1 u.t., where Fine-grain retiming is allowed. Do this by inspection (manually).



- 2 loop,
  - Red loop, 3 adders & 2 multipliers, 4 delays,  $3 \times 1 + 2 \times 2 = 7$   
 Loop bound =  $7/4 = 1.75$  u.t.
  - Green loop, 4 adders & 3 multipliers, 8 delays,  $4 \times 1 + 3 \times 2 = 10$   
 Loop bound =  $10/8 = 1.25$  u.t.
 Iteration bound =  $\max(1.75, 1.25) = 1.75$  u.t.
- Red path, 3 adders & 2 multipliers,  $3 \times 1 + 2 \times 2 = 7$   
 Critical path time = 7 u.t.
- Pipeline from IN with 2 delays. After retiming, the result is shown below.

 


- Since iteration bound is greater 1 u.t. (1.75 u.t.), it's unable to use pipelining or retiming only to achieve a critical path of 1 u.t.

3. The two IIR filter DFGs shown below are equivalent.

(a) Prove the two circuits are equivalent.

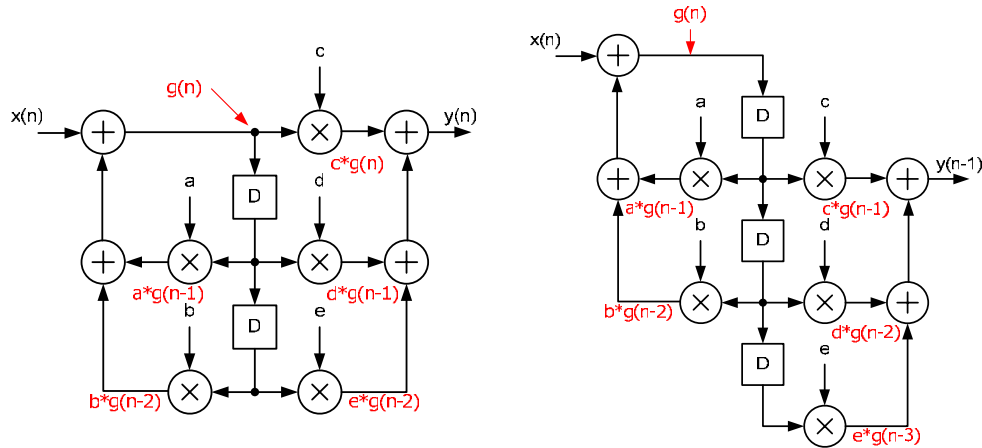(b) Transform the left circuit to the right circuit by pipelining and/or retiming.



(a) Let  $g(n)$  be the results indicated in these figures.

A. Left graph:

$$g(n) = x(n) + ag(n-1) + bg(n-2)$$

$$y(n) = cg(n) + dg(n-1) + e(g-2)$$

B. Right graph:

$$g(n) = x(n) + ag(n-1) + bg(n-2)$$

$$y(n-1) = cg(n-1) + dg(n-2) + e(g-3) \rightarrow y(n) = cg(n) + dg(n-1) + e(g-2)$$

According to A & B, two circuits are equivalent.

(b) Pipeline from  $x(n)$  with 1 delays. Take blue lines as one node and green lines as another. Combine 2 individual delays between blue node and green node. Then the final result is obtained.

